

# Binary to gray code converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_binary_to_gray;
4     reg [3:0] bin;
5     wire [3:0] gray;
6
7     binary_to_gray uut (.bin(bin),
8         .gray(gray));
9
10    initial begin
11        $monitor("Time=%0t | Binary=%b |
12        Gray=%b", $time, bin, gray);
13        bin=4'b0000;#10;
14        bin=4'b0001;#10;
15        bin=4'b0010;#10;
16        bin=4'b0100;#10;
17        bin=4'b1111;#10;
18        $finish;
19    end
20 endmodule
```

```
1 // Code your design here
2 module binary_to_gray (
3     input [3:0] bin,
4     output [3:0] gray
5 );
6     assign gray[3] = bin[3];
7     assign gray[2] = bin[3] ^ bin[2];
8     assign gray[1] = bin[2] ^ bin[1];
9     assign gray[0] = bin[1] ^ bin[0];
10 endmodule
11
```

## Output:

Time=0 | Binary=0000 | Gray=0000  
Time=10 | Binary=0001 | Gray=0001  
Time=20 | Binary=0010 | Gray=0011  
Time=30 | Binary=0100 | Gray=0110  
Time=40 | Binary=1111 | Gray=1000

# Gray to binary code converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_gray_to_binary;
4     reg [3:0] gray;
5     wire [3:0] bin;
6
7     gray_to_binary uut (.gray(gray),
8 .bin(bin));
9
10    initial begin
11        $monitor("Time=%0t | Gray=%b |
12 Binary=%b", $time, gray, bin);
13        gray=4'b0000;#10;
14        gray=4'b0001;#10;
15        gray=4'b0010;#10;
16        gray=4'b0011;#10;
17        gray=4'b0100;#10;
18        gray=4'b0101;#10;
19        gray=4'b0110;#10;
20        gray=4'b1111;#10;
21        $finish;
22    end
23 endmodule
```

```
1 // Code your design here
2 module gray_to_binary (
3     input [3:0] gray,
4     output [3:0] bin
5 );
6     assign bin[3] = gray[3];
7     assign bin[2] = gray[3] ^ gray[2];
8     assign bin[1] = bin[2] ^ gray[1];
9     assign bin[0] = bin[1] ^ gray[0];
10 endmodule
```

## Output:

Time=0 | Gray=0000 | Binary=0000

Time=10 | Gray=0001 | Binary=0001

Time=20 | Gray=0010 | Binary=0011

Time=30 | Gray=0011 | Binary=0010

Time=40 | Gray=0100 | Binary=0111

Time=50 | Gray=0101 | Binary=0110

Time=60 | Gray=0110 | Binary=0100

Time=70 | Gray=1111 | Binary=1010

# Binary to BCD code converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_binary_to_bcd;
4     reg [3:0] bin;
5     wire [3:0] ones,tens;
6
7     binary_to_bcd_gate uut(.bin(bin),
8     .ones(ones),.tens(tens));
9
10    initial begin
11        $monitor("bin=%b => tens=%d ones=%d",
12        bin, tens, ones);
13        bin = 4'd0;#10;
14        bin = 4'd5;#10;
15        bin = 4'd7;#10;
16        bin = 4'd9;#10;
17        bin = 4'd10;#10;
18        bin = 4'd12;#10;
19        bin = 4'd15;#10;
20        $finish;
21    end
22 endmodule
```

```
1 // Code your design here
2 module binary_to_bcd_gate(input[3:0]bin,
3 output [3:0]ones,output[3:0] tens);
4     wire [3:0]b;
5     assign b=bin;
6
7     assign tens[0] =(b[3] & b[2]) | (b[3] &
8     b[1]);
9     assign tens[1] =(b[3] & b[2] & ~b[1]) |
10    (b[3] & b[1] & b[0]);
11    assign tens[2] =0;
12    assign tens[3] =0;
13
14    assign ones= b-(tens*4'd10);
15 endmodule
```

## Output:

bin=0000 => tens= 0 ones= 0

bin=0101 => tens= 0 ones= 5

bin=0111 => tens= 0 ones= 7

bin=1001 => tens= 0 ones= 9

bin=1010 => tens= 1 ones= 0

bin=1100 => tens= 3 ones=14

bin=1111 => tens= 3 ones= 1

# BCD to binary code converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_bcd_to_binary;
4     reg [7:0]bcd;
5     wire [6:0]bin;
6
7     bcd_to_binary uut(.bcd(bcd), .bin(bin));
8
9     initial begin
10         $monitor("BCD=%b -> Binary=%d", bcd,
11 bin);
12         bcd = 8'b0000_0101;#10;
13         bcd = 8'b0001_0010;#10;
14         bcd = 8'b0010_0101;#10;
15         bcd = 8'b0101_1001;#10;
16         bcd = 8'b1001_1001;#10;
17         bcd = 8'b1010_1010;#10;
18
19         $finish;
20     end
21 endmodule
```

```
1 // Code your design here
2 module bcd_to_binary(input [7:0]bcd,
3 output [6:0] bin);
4     assign bin =(bcd[7:4]*4'd10)+ bcd[3:0];
5 endmodule
6
```

## Output:

BCD=00000101 -> Binary= 5

BCD=00010010 -> Binary= 12

BCD=00100101 -> Binary= 25

BCD=01011001 -> Binary= 59

BCD=10011001 -> Binary= 99

BCD=10101010 -> Binary=110

# Excess 3 to BCD converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_excess3_to_bcd;
4     reg [3:0]ex3;
5     wire [3:0]bcd;
6
7     excess3_to_bcd uut(.ex3(ex3),
8 .bcd(bcd));
9
10    initial begin
11        $monitor("Excess-3 = %b, BCD = %b",
12 ex3, bcd);
13 ex3 = 4'b0011;#10;
14 ex3 = 4'b0010;#10;
15 ex3 = 4'b0001;#10;
16 ex3 = 4'b0100;#10;
17 ex3 = 4'b0101;#10;
18 ex3 = 4'b0110;#10;
19 ex3 = 4'b0111;#10;
20 $finish;
21 end
22 endmodule
```

```
1 // Code your design here
2 module excess3_to_bcd(input[3:0]ex3,
3 output [3:0]bcd);
4     assign bcd =ex3-4'd3;
5 endmodule
```

## Output:

Excess-3 = 0011, BCD = 0000

Excess-3 = 0010, BCD = 1111

Excess-3 = 0001, BCD = 1110

Excess-3 = 0100, BCD = 0001

Excess-3 = 0101, BCD = 0010

Excess-3 = 0110, BCD = 0011

Excess-3 = 0111, BCD = 0100

# BCD to excess 3 converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_bcd_to_excess3;
4     reg [3:0]bcd;
5     wire [3:0]ex3;
6
7     bcd_to_excess3 uut(.bcd(bcd),
8 .ex3(ex3));
9
10    initial begin
11        $monitor("BCD = %b, Excess-3 = %b",
12 bcd, ex3);
13        bcd = 4'b0000;#10;
14        bcd = 4'b0001;#10;
15        bcd = 4'b0010;#10;
16        bcd = 4'b0011;#10;
17        bcd = 4'b0100;#10;
18        bcd = 4'b0101;#10;
19        bcd = 4'b0110;#10;
20        bcd = 4'b0111;#10;
21        bcd = 4'b1000;#10;
22        bcd = 4'b1001;#10;
23        bcd = 4'b1010;#10;
24        bcd = 4'b1011;#10;
25        bcd = 4'b1100;#10;
26        bcd = 4'b1101;#10;
27        bcd = 4'b1110;#10;
28        bcd = 4'b1111;#10;
29        $finish;
30    end
31 endmodule
```

```
1 // Code your design here
2 module bcd_to_excess3(input [3:0]bcd,
3 output [3:0]ex3);
4     assign ex3 = bcd+4'd3;
5 endmodule
```

## Output:

BCD = 0000, Excess-3 = 0011  
BCD = 0001, Excess-3 = 0100  
BCD = 0010, Excess-3 = 0101  
BCD = 0011, Excess-3 = 0110  
BCD = 0100, Excess-3 = 1000  
BCD = 0101, Excess-3 = 1001  
BCD = 0110, Excess-3 = 1010  
BCD = 0111, Excess-3 = 1011  
BCD = 1000, Excess-3 = 1100  
BCD = 1001, Excess-3 = 1101  
BCD = 1010, Excess-3 = 1110  
BCD = 1011, Excess-3 = 1111  
BCD = 1100, Excess-3 = 0000  
BCD = 1101, Excess-3 = 0001  
BCD = 1110, Excess-3 = 0010  
BCD = 1111, Excess-3 = 0011

# ASCII to binary code converter

```
1 // Code your testbench here
2 // or browse Examples
3 module tb_ascii_to_binary;
4     reg [7:0]ascii;
5     wire [3:0]binary;
6
7     ascii_to_binary uut(.ascii(ascii),
8     .binary(binary));
9
10    initial begin
11        $monitor("ASCII = %d (%c), Binary =
12        %d", ascii, ascii, binary);
13        ascii = 8'd48;#10;
14        ascii = 8'd49;#10;
15        ascii = 8'd50;#10;
16        ascii = 8'd57;#10;
17        ascii = 8'd52;#10;
18        ascii = 8'd53;#10;
19
20        $finish;
21    end
22 endmodule
```

```
1 // Code your design here
2 module ascii_to_binary(input [7:0] ascii,
3     output [3:0] binary);
4     assign binary =ascii-8'd48;
5 endmodule
```

## Output:

ASCII = 48 (0), Binary = 0  
ASCII = 49 (1), Binary = 1  
ASCII = 50 (2), Binary = 2  
ASCII = 57 (9), Binary = 9  
ASCII = 52 (4), Binary = 4  
ASCII = 53 (5), Binary = 5